
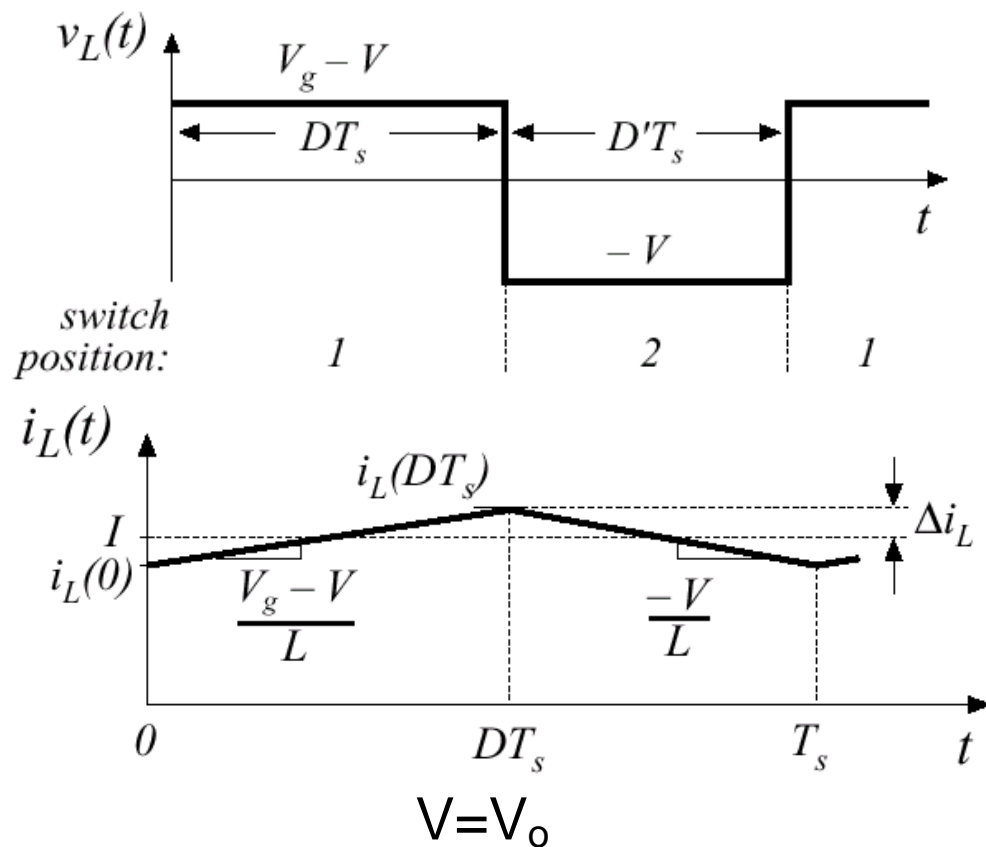


INDUCTOR CURRENT RIPPLE


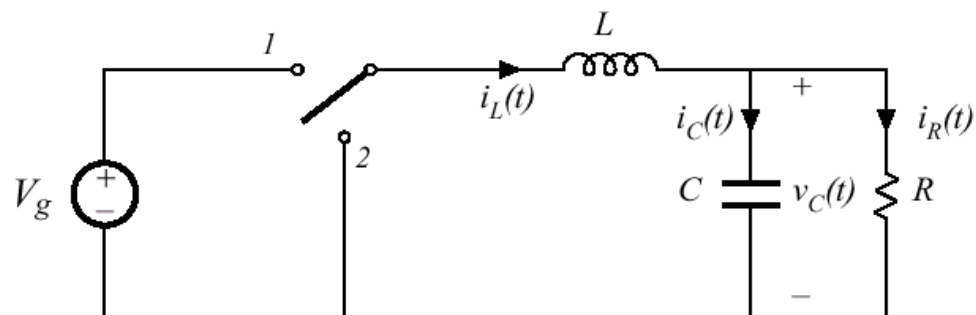


$$2\Delta i_L = D(V_g - V_o)/f_s L \leq \Delta i_{Lpp}$$

\Downarrow

$$L \geq D(V_g - V_o)/(f_s \Delta i_{Lpp})$$

CAPACITOR VOLTAGE RIPPLE

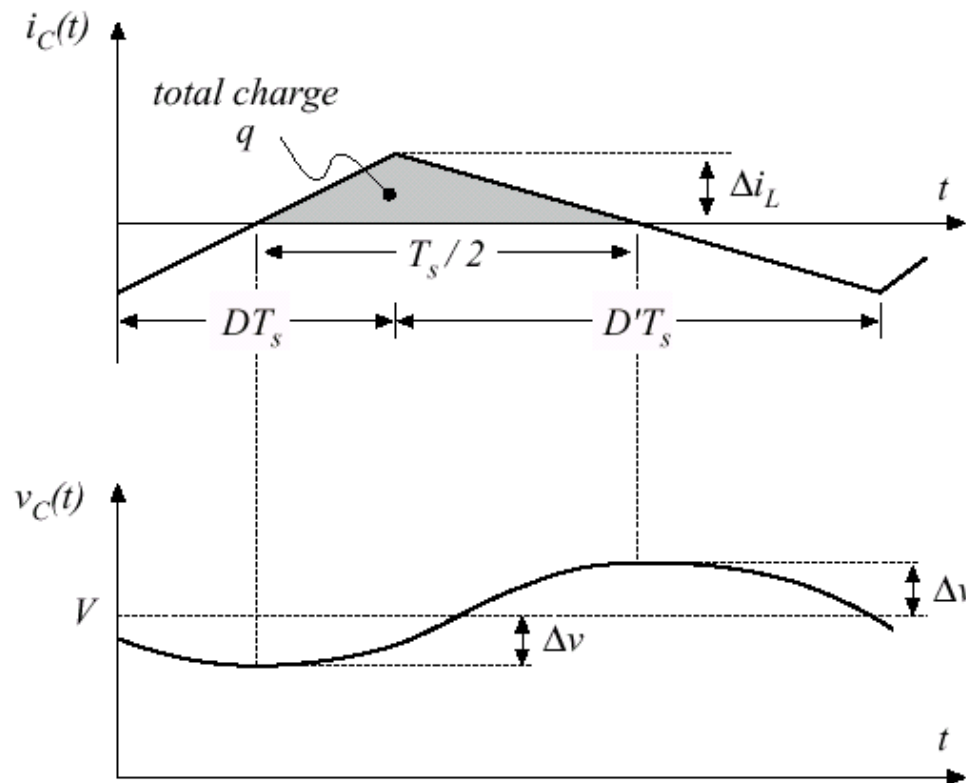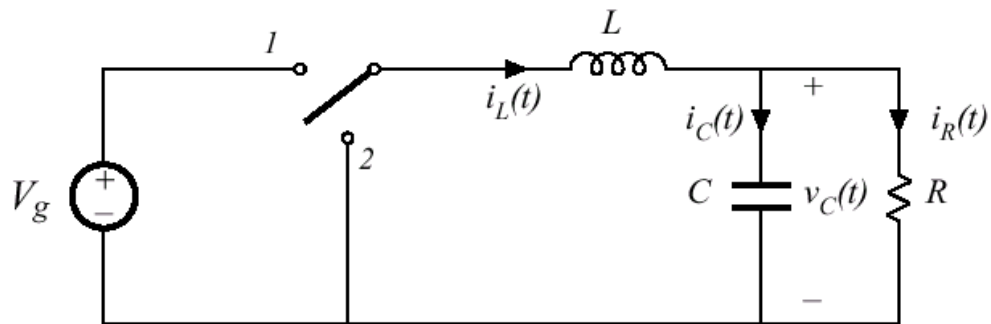

$$q = C \, 2\Delta v = \Delta i_{Lpp} / (8f_s)$$

$$2\Delta v \leq \Delta v_{opp}$$



⇓

$$C \geq \Delta i_{Lpp} / (8f_s \Delta v_{opp})$$

⇓

$$C \geq \Delta i_{Lpp} / (\Delta v_{opp} 8f_s)$$

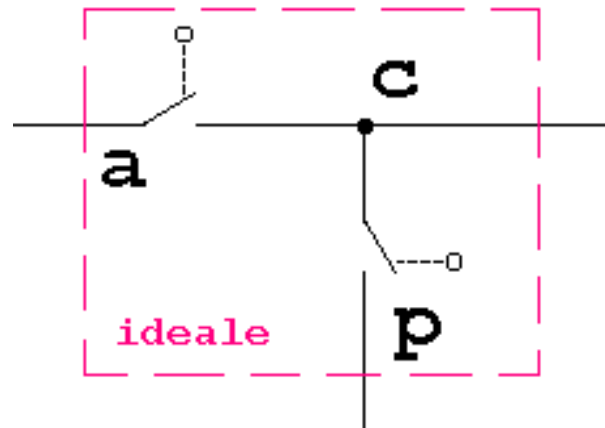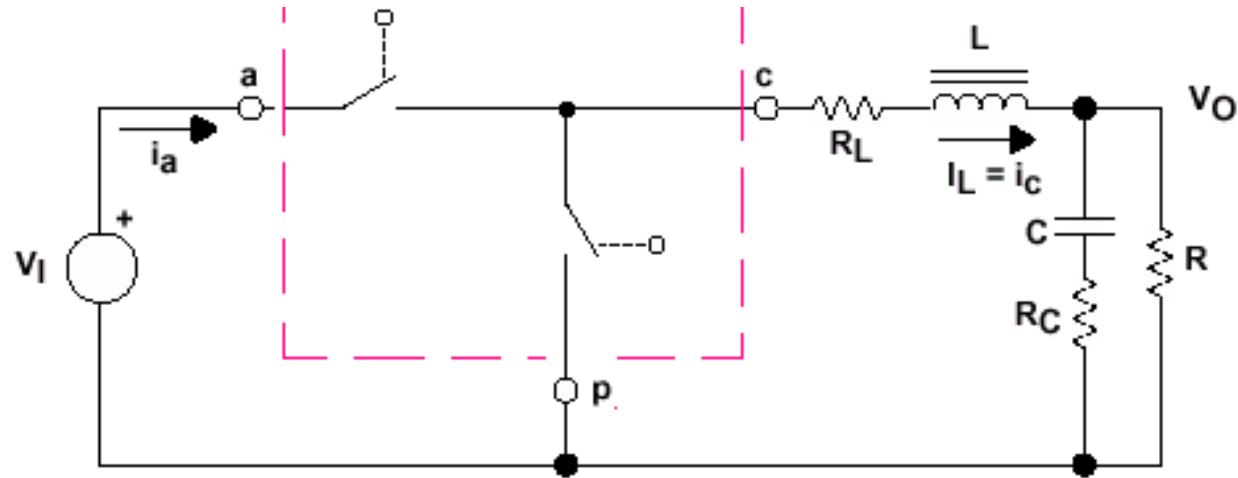
$$L \geq D(V_g - V) / (f_s \Delta i_{Lpp})$$



$$i_c = i_a + i_p \quad V_{ap} = V_{ac} + V_{cp}$$

$$\langle i_a \rangle = d \times \langle i_c \rangle$$
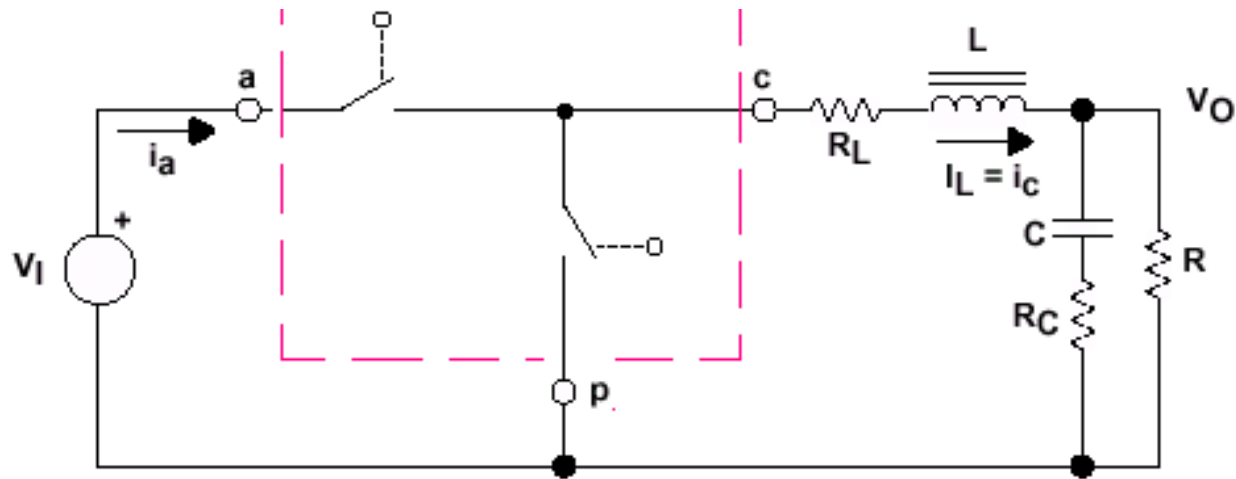
$$\langle V_{cp} \rangle = d \times \langle V_{ap} \rangle$$



a regime (dc)

$$I_a = D \cdot I_c$$


$$V_{cp} = D \cdot V_{ap}$$

alle variazioni (ac)

$$\hat{I}_a = D \cdot \hat{I}_c + I_c \cdot \hat{d}$$


$$\hat{V}_{cp} = D \cdot \hat{V}_{ap} + V_{ap} \cdot \hat{d}$$

buck-boost

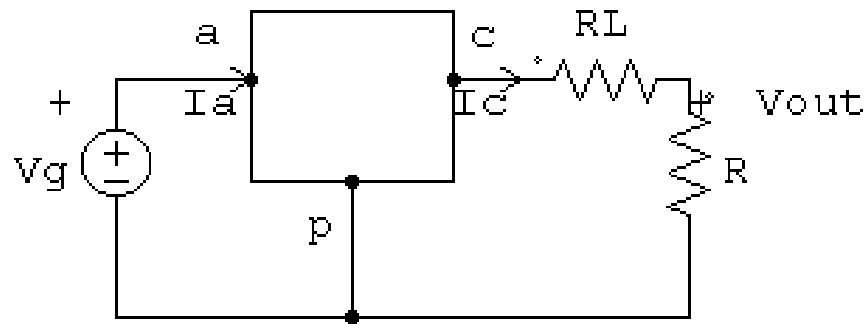

modello statico

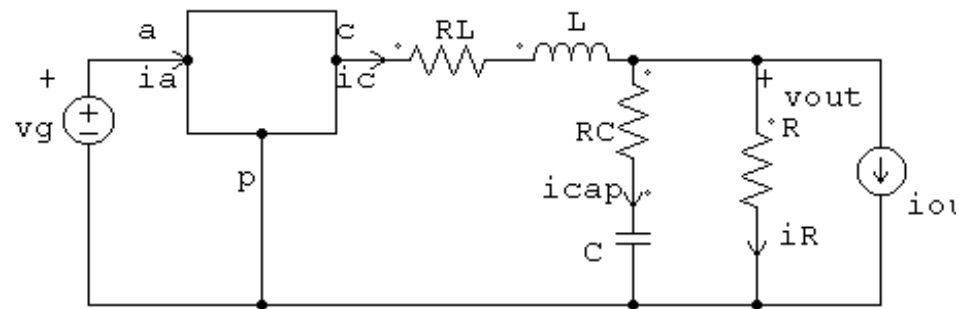LKT1: $V_g = V_{ap}$
 LKT2: $V_{cp} = R_L \cdot I_c + V_{out}$
 LKC: $I_{out} = I_c$
 EQC1: $V_{out} = R \cdot I_{out}$
 EQC2: $I_a = D \cdot I_c$
 EQC3: $V_{cp} = D \cdot V_{ap}$
 EQC3: $V_{cp} = D \cdot V_{ap}$



modello dinamico

lkt1: $V_g = V_{ap}$
 lkt2: $V_{cp} = (R_L + s \cdot L) \cdot i_c + v_{out}$
 lkt3: $v_{out} = (R_C + 1/(s \cdot C)) \cdot i_{cap}$
 lkc: $i_c = i_{cap} + i_R + i_o$
 eqc1: $v_{out} = R \cdot i_R$
 eqc2: $i_a = D \cdot i_c + I_c \cdot d$
 eqc3: $v_{cp} = D \cdot v_{ap} + V_{ap} \cdot d$