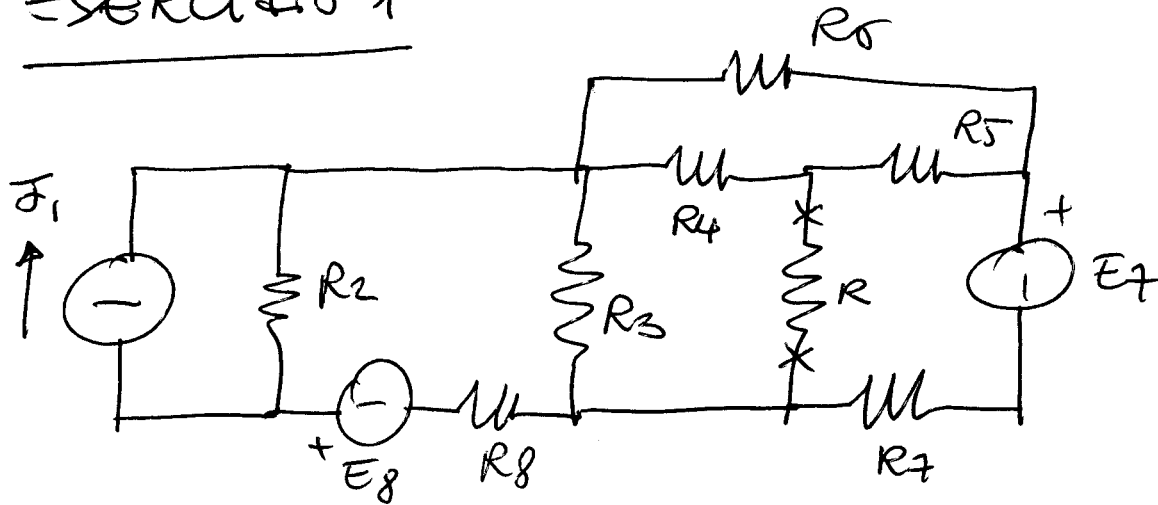


ESERCIZIO 1



$$R_4 = R_5 = R_6 = 3\Omega$$

$$R_1 = R_8 = R_2 = 2\Omega$$


$$R_3 = 4\Omega$$

$$E_7 = 4V$$

$$E_8 = 22V$$

$$J_1 = 11A$$

• tensione a vuoto

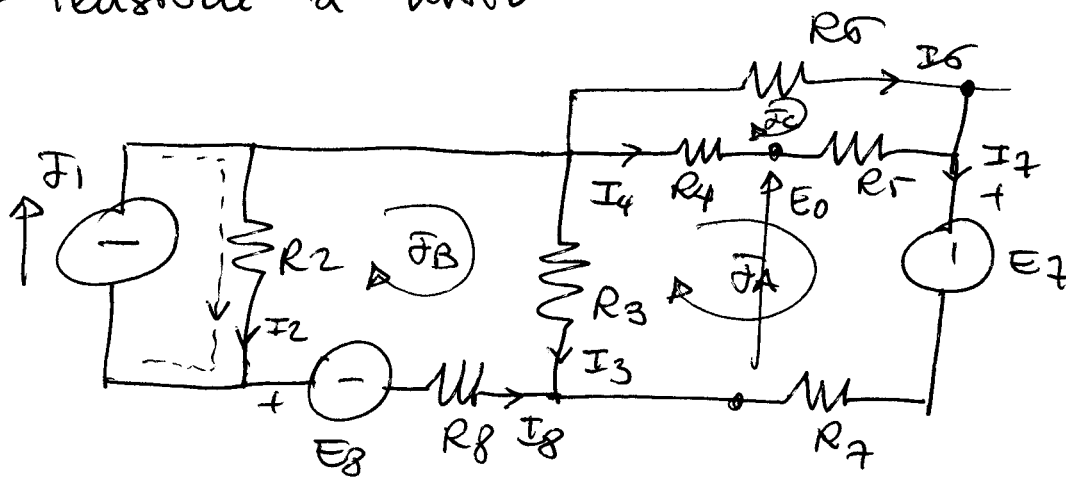

$$I_2 = J_1 - J_B$$

$$I_8 = -J_B$$

$$I_3 = J_B - J_A$$

$$I_4 = J_A - J_C$$

$$I_6 = J_C$$

$$I_7 = J_A$$


$$\begin{cases} E_8 + R_2(J_1 - J_B) - R_3(J_B - J_A) + R_8(-J_B) = 0 \\ E_7 + (R_4 + R_5)(J_A - J_C) - R_3(J_B - J_A) + R_7 J_A = 0 \\ (R_4 + R_5)(J_A - J_C) = R_5 J_C \end{cases}$$

$$\begin{bmatrix} R_3 & (-R_2 - R_3 - R_8) & 0 \\ (R_4 + R_5 + R_3 + R_7) & -R_3 & (-R_4 - R_5) \\ R_4 + R_5 & 0 & -R_4 - R_5 - R_5 \end{bmatrix} \begin{bmatrix} J_A \\ J_B \\ J_C \end{bmatrix} = \begin{bmatrix} -E_8 - R_2 J_1 \\ -E_7 \\ 0 \end{bmatrix}$$


$$J_A = 3A \quad J_B = 7A \quad J_C = 2A$$

$$E_0 = R_5 I_4 + R_7 I_7 + E_7 = 3 \cdot (3 - 2) + 2 \cdot (3) + 4 = 13V$$


• Resistenze equivalenti:

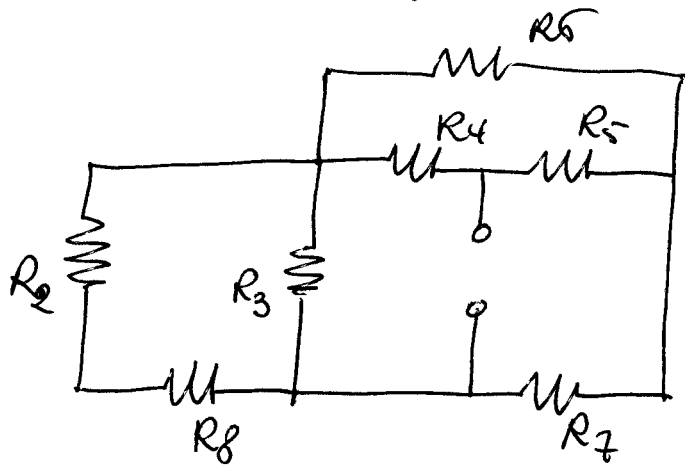

$\sim >$

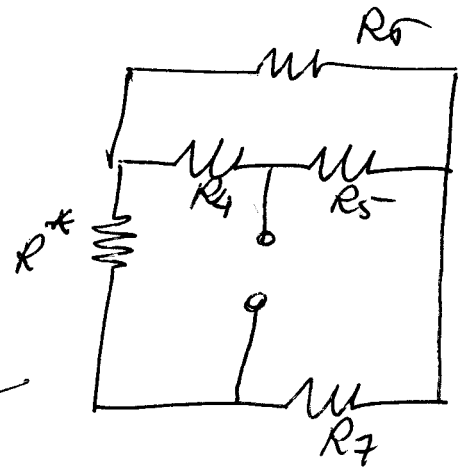

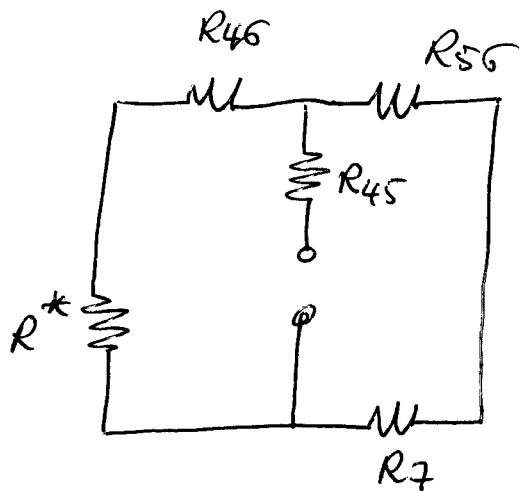
$$R^* = (R_2 + R_8) \parallel R_3 = 2 \Omega$$



$$R_{46} = R_{56} = R_{45} = 1 \Omega$$

$$R_{eq} = (R_{45} + R^*) \parallel (R_{56} + R_7) + R_{46} = 2.5 \Omega$$


da cui

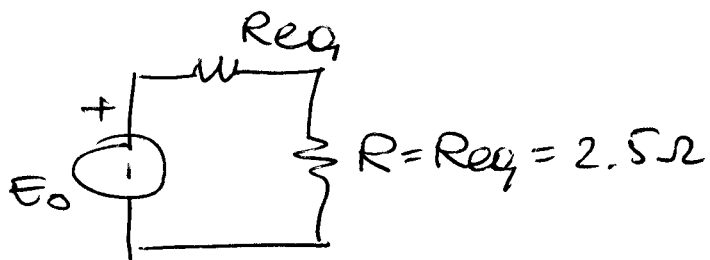

per avere il massimo
trasferimento di potenza.

$$P_R = R \left(\frac{E_0}{R + R_{eq}} \right)^2 = 2.5 \left(\frac{13}{5} \right)^2 = 16.9 \text{ W}$$

ÜBUNG 2

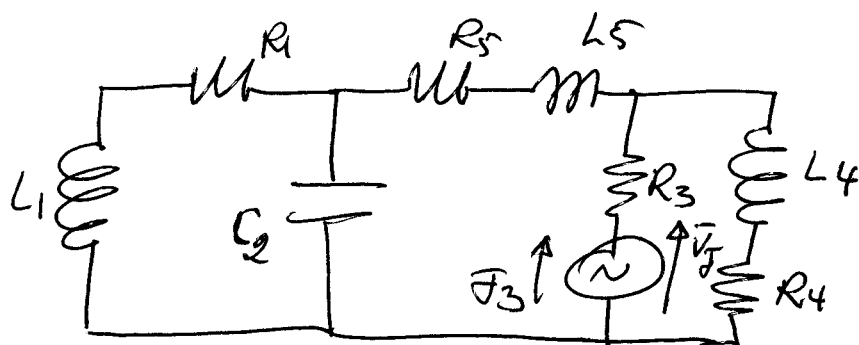

$$\vec{f}_3(t) = 100 \sin(10t + \pi/4)$$

$$L_1 = 0.1 \text{ H}$$

$$R_3 = 5 \Omega$$

$$L_5 = 0.3 \text{ H}$$

$$R_4 = 3 \Omega$$

$$L_4 = 0.2 \text{ H}$$

$$R_5 = 2 \Omega$$

$$C_2 = 0.1 \text{ F}$$

$$R_1 = 1 \Omega$$

$$\vec{F}_3 = \frac{100}{\sqrt{2}} e^{j\pi/4} = 50(1+j)$$

$$X_1 = 10 \cdot 0.1 = 1 \Omega$$

$$X_5 = 3 \Omega$$

$$X_4 = 2 \Omega$$

$$X_2 = \frac{1}{10 \cdot 0.1} = 1 \Omega$$

$$\hat{Z}_{eq} = [(R_1 + jX_1) \parallel (-jX_2) + R_5 + jX_5] \parallel (R_4 + jX_4) + R_3 = 6.5 + j$$

$$\vec{V}_J = \hat{Z}_{eq} \cdot \vec{F}_3 = 100 \cdot (2.75 + j3.75) \approx 465 e^{j54^\circ}$$

$$\vec{V}_J(t) = 465 \sqrt{2} \sin(10t + 0.938) \quad 0.938 \text{ rad} \Rightarrow 54^\circ$$